

Assignment - 1


Analog Electronics

R1 VCVS

The parameter is g-parameter.

The dependent sources are (I_1, V_2)

and independent sources are (V_1, I_2)

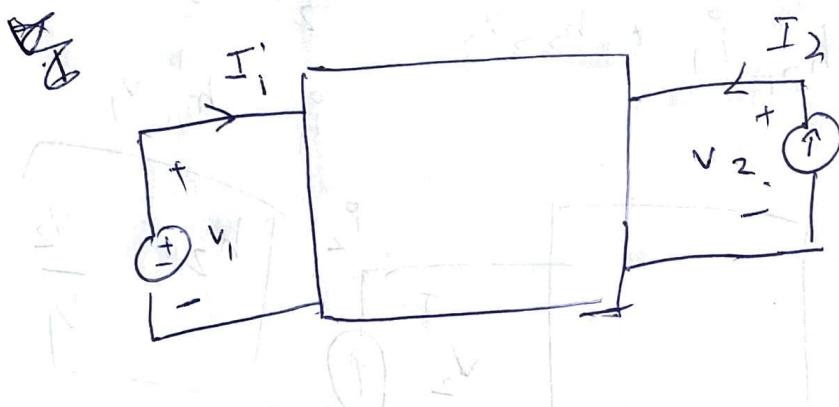

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$


when $I_2 = 0$ [acts like VCVS circuit]

$$I_1 = g_{11} V_1 \quad ; \quad V_2 = g_{21} V_1$$

$$\boxed{g_{11} = \frac{I_1}{V_1} = 0}$$

$$\boxed{g_{21} = \frac{V_2}{V_1}}$$

~~when $V_1 = 0$~~

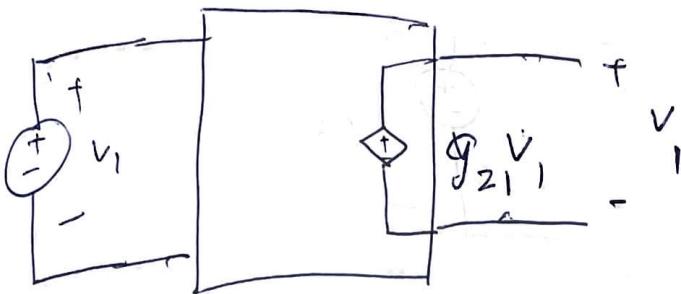

when $V_1 = 0$

$$I_1 = g_{12} I_2 \quad ; \quad V_2 = g_{22} I_2$$

$$g_{12} = -\frac{I_1}{I_2} = 0 \quad ; \quad g_{22} = \frac{V_2}{I_2} = 0$$

$$G_1 = \begin{bmatrix} \frac{I_1}{V_1} & \frac{I_1}{I_2} \\ \frac{V_2}{V_1} & \frac{V_2}{I_2} \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = G_1 \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$G_2 = \begin{bmatrix} 0 & 0 \\ \frac{V_2}{V_1} & 0 \end{bmatrix}$$

VCCS


$g_{11}, g_{12}, g_{22} = 0$ since
it is a VCVS

The para pector is γ -parameters

The Dependent sources are (I_1, I_2) and independent
sources are (V_1, V_2)

$$I_1 = \gamma_{11} V_1 + \gamma_{12} V_2$$
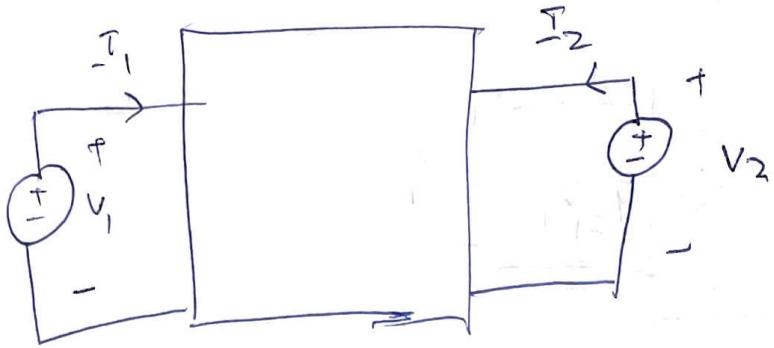
$$I_2 = \gamma_{21} V_1 + \gamma_{22} V_2$$



when $V_1 = 0$


$$I_1 = \gamma_{12} V_2 \Rightarrow \gamma_{12} = \frac{I_1}{V_2} = 0$$

$$I_2 = \gamma_{22} V_2 \Rightarrow \gamma_{22} = \frac{I_2}{V_2} = 0$$

when $V_2 = 0$

$$I_1 = \gamma_{11} V_1 ; \quad I_2 = \gamma_{21} V_1$$
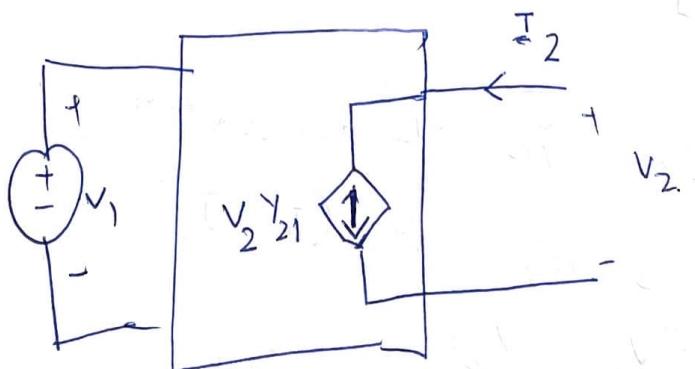
$$\gamma_{11} = \frac{I_1}{V_1} = 0 ; \quad \gamma_{21} = \frac{I_2}{V_1}$$



VCCS

$$\gamma = \begin{bmatrix} 0 & 0 \\ \frac{I_2}{V_1} & 0 \end{bmatrix}$$

CCVS

The parameter is Z - parameters. The dependent sources are $Z(v_1, v_2)$ and independent sources are (I_1, I_2)

$$v_1 = Z_{11} I_1 + Z_{12} I_2$$

$$v_2 = Z_{21} I_1 + Z_{22} I_2$$

when $I_1 = 0$

$$v_1 = Z_{12} I_2 ; \quad v_2 = Z_{22} I_2$$


$$Z_{12} = \frac{v_1}{I_2} = 0 ; \quad Z_{22} = \frac{v_2}{I_2} = 0$$

when $I_2 = 0$


$$v_1 = Z_{11} I_1 \Rightarrow Z_{11} = \frac{v_1}{I_1} = 0$$

$$v_2 = Z_{21} I_1 \Rightarrow Z_{21} = \frac{v_2}{I_1}$$
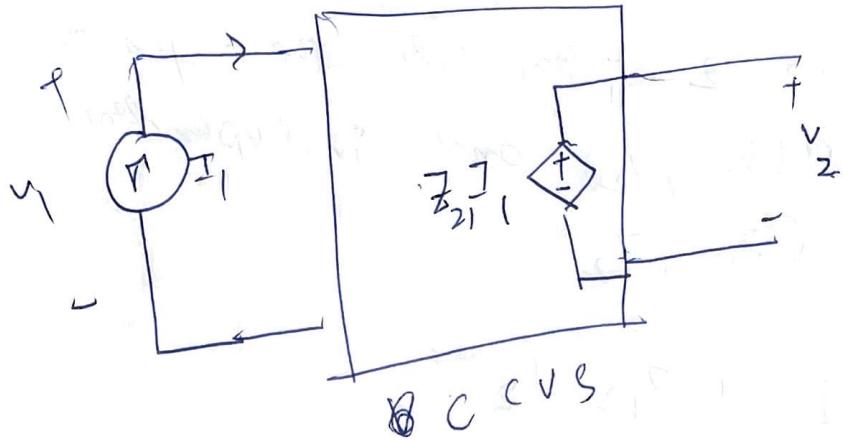
$$Z = \begin{bmatrix} \frac{v_1}{I_1} & \frac{v_1}{I_2} \\ \frac{v_2}{I_1} & \frac{v_2}{I_2} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \frac{v_2}{I_1} & 0 \end{bmatrix}$$



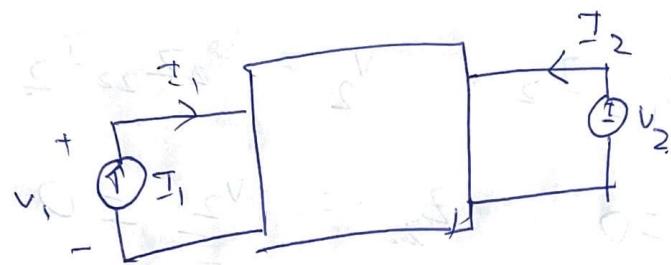~~CCCS~~
The parameters used is h-parameters



$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\text{when } I_1 = 0$$

$$V_1 = h_{12} V_2 ; \quad I_2 = h_{22} V_2$$




$$\therefore h_{12} = \frac{V_1}{V_2} = 0 ; \quad h_{22} = \frac{I_2}{V_2} = 0$$

$$\text{when } V_2 = 0$$

$$V_1 = h_{11} I_1 ; \quad I_2 = h_{21} I_1$$

$$\frac{V_1}{h_{11}} = \frac{I_1}{I_1} = 0 ; \quad h_{21} = \frac{I_2}{I_1}$$
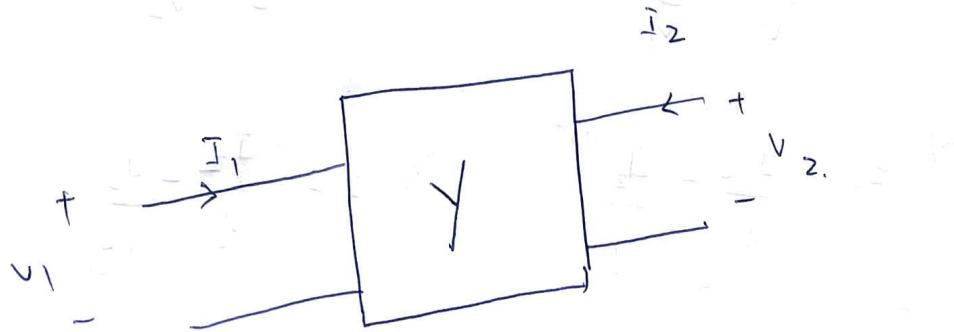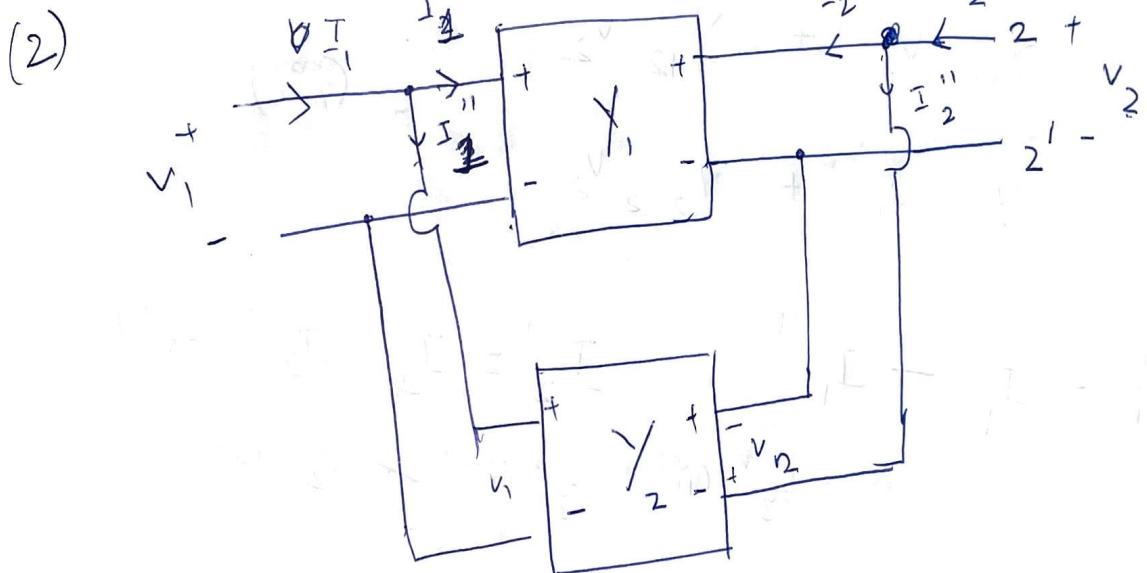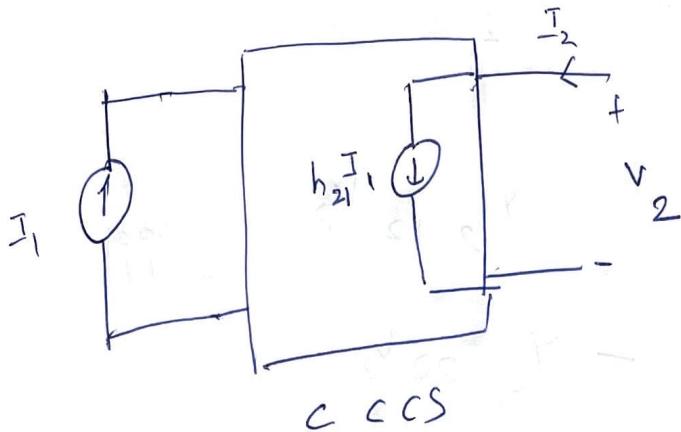
$$H = \begin{bmatrix} v_1 \\ \bar{v}_1 \\ \bar{v}_2 \\ \bar{v}_2 \\ I_2 \\ \bar{I}_1 \end{bmatrix} \quad \Rightarrow \quad \begin{bmatrix} 0 \\ \bar{I}_2 \\ \bar{I}_1 \\ 0 \end{bmatrix}$$



(1)

$$I_1' = Y_{1,11} V_1 + Y_{1,12} \frac{V_2}{V_2} - (1)$$

$$I_2' = Y_{1,21} V_1 + Y_{2,22} \frac{V_2}{V_2}$$

$$I_1'' = Y_{2,11} V_1 - Y_{2,12} \frac{V_2}{V_2} - (1)$$

$$-I_2'' = Y_{2,21} V_1 - Y_{2,22} \frac{V_2}{V_2}$$

$$I_1 = Y_{1,1} V_1 + Y_{1,2} \frac{V_2}{V_2} + (1)$$

$$I_2 = Y_{2,1} V_1 + Y_{2,2} \frac{V_2}{V_2}$$

$$I_1' = I_1 - I_1'' \quad I_2' = I_2 - I_2'' \quad (1)$$

solving $\underline{\underline{Y}}_{1,11}^{(1)}, \underline{\underline{Y}}_{2,11}^{(1)}, \underline{\underline{Y}}_{1,22}^{(1)}, \underline{\underline{Y}}_{2,22}^{(1)}$

$$Y_{1,11} = \frac{I_1'}{V_1} - \frac{I_1''}{V_1}$$

$$Y_{1,12} = \frac{I_1'}{V_2} - \frac{I_1''}{V_2}$$

$$Y_{1,21} = \frac{I_2'}{V_1} - \frac{I_2''}{V_1}$$

$$Y_{1,22} = \frac{I_2'}{V_2} - \frac{I_2''}{V_2}$$

$$Y_{2,11} = \frac{I_1''}{V_1}, \quad Y_{2,12} = -\frac{I_1''}{V_2}$$

$$y_{2,21} = -\frac{I_2}{v_1} \quad y_{2,22} = \frac{I_2}{v_2}$$

$$y_{1,11} = \frac{I_1}{v_1} - y_{2,11}$$

$$y_{1,12} = \frac{I_1}{v_2} + y_{2,12}$$

$$y_{2,21} = \frac{I_2}{v_1} + y_{2,21}$$

$$y_{1,22} = \frac{I_2}{v_2} - y_{2,22}$$

$$y_{1,11} + y_{2,11} = \frac{I_1}{v_1}$$

$$y_{1,12} - y_{2,12} = \frac{I_1}{v_2}$$

$$y_{1,21} - y_{2,21} = \frac{I_2}{v_1}$$

$$y_{1,22} + y_{2,22} = \frac{I_2}{v_2}$$


$$y_{11} = y_{1,11} + y_{2,11}$$

$$y_{12} = y_{1,12} - y_{2,12}$$

$$y_{21} = y_{1,21} - y_{2,21}$$

$$y_{22} = y_{1,22} + y_{2,22}$$

(b)

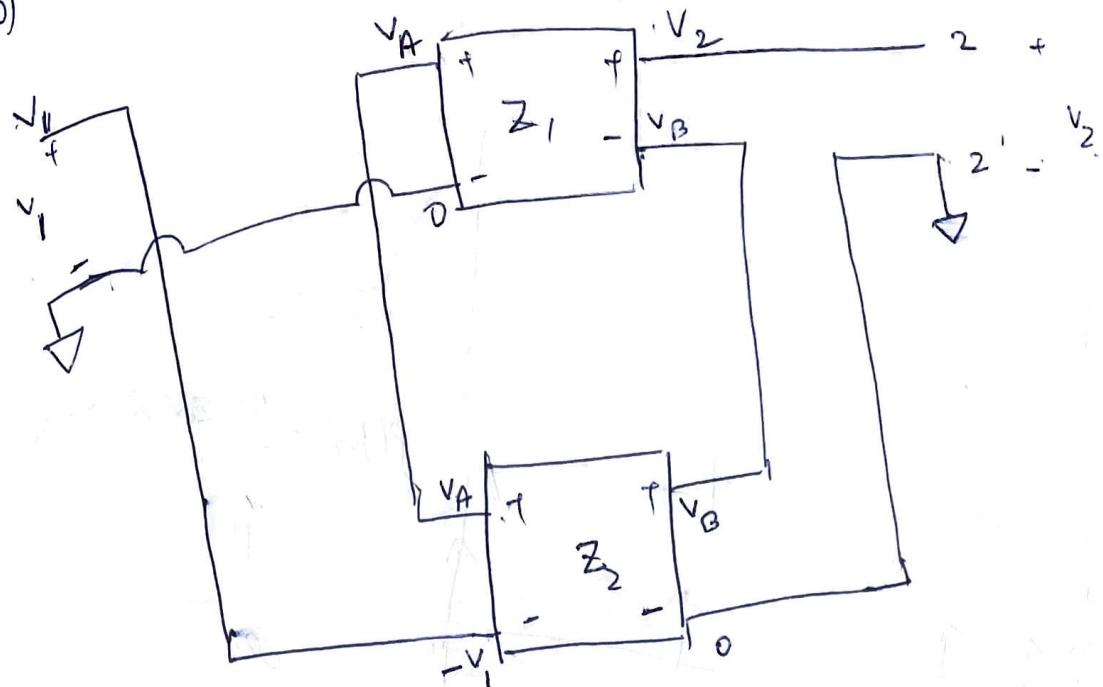

for Z_1 the input voltage is V_A and output voltage is $(V_2 - V_B)$

for Z_2 the input voltage is $(V_A - V_1)$ and output voltage is V_B

for Z_1

$$V_A - 0 = Z_{1,11} I_1 + Z_{1,12} I_2 \quad (i)$$

$$V_2 - V_B = Z_{1,21} I_1 + Z_{1,22} I_2$$

for Z_2

$$V_A - V_1 = -Z_{2,11} I_1 + Z_{2,12} I_2 \quad (ii)$$

$$V_B = -Z_{2,21} I_1 + Z_{2,22} I_2$$

of 2

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2)$$

On solving eqn (1), (2) Δ (19)

$$V_2 = \cancel{Z_{12}} Z_{1,21} I_1 + Z_{1,22} I_2 + V_B$$

$$V_2 = Z_{1,21} I_1 + Z_{1,22} I_2 - Z_{2,21} I_1 + Z_{2,22} I_2$$

$$V_2 = (Z_{1,21} - Z_{2,21}) I_1 + (Z_{1,22} + Z_{2,22}) I_2$$

$$V_1 = Z_{2,11} I_1 - Z_{2,12} I_2 + V_A$$

$$V_1 = Z_{2,11} I_1 - Z_{2,12} I_2 + Z_{1,11} I_1 + Z_{1,12} I_2$$

$$V_1 = (Z_{2,11} + Z_{1,11}) I_1 + (Z_{1,12} - Z_{2,12}) I_2$$

$$\therefore \begin{cases} V_1 = (Z_{2,11} + Z_{1,11}) I_1 + (Z_{1,12} - Z_{2,12}) I_2 \\ V_2 = (Z_{1,21} - Z_{3,21}) I_1 + (Z_{1,22} + Z_{2,22}) I_2 \end{cases}$$


on comparing eqⁿ (ii) and (vi) with (iii)

$$Z_{11} = Z_{1,11} + Z_{2,11}$$

$$Z_{12} = Z_{1,12} - Z_{2,12}$$

$$Z_{21} = Z_{1,21} - Z_{2,21}$$


$$Z_{22} = Z_{1,22} + Z_{2,22}$$


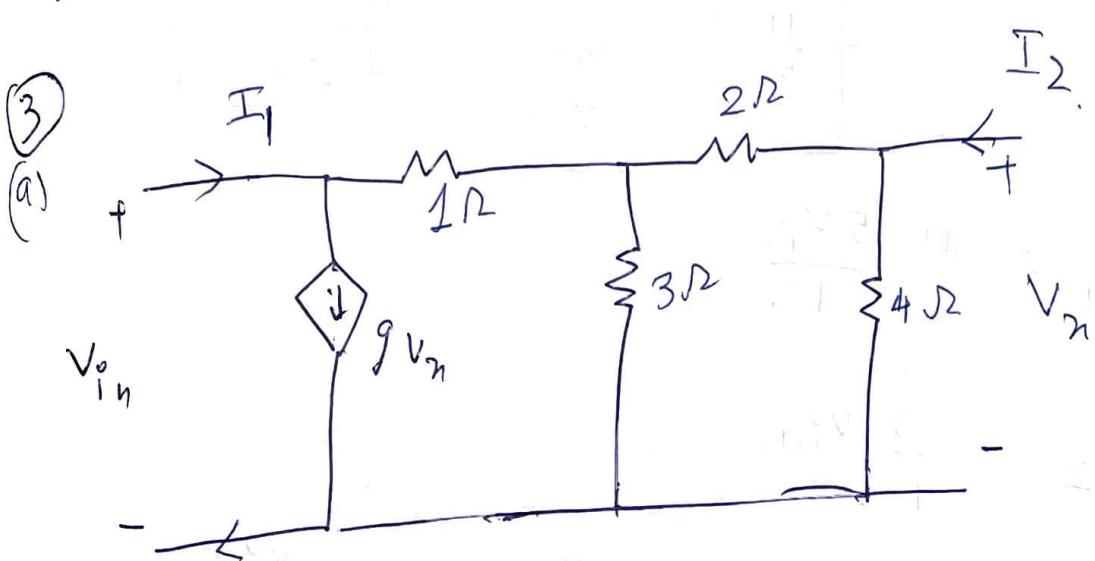


$$I_1 = \gamma_{11} V_{1n} + \gamma_{12} V_n$$

$$I_2 = \gamma_{21} V_{1n} + \gamma_{22} V_n$$

when $V_n = 0$

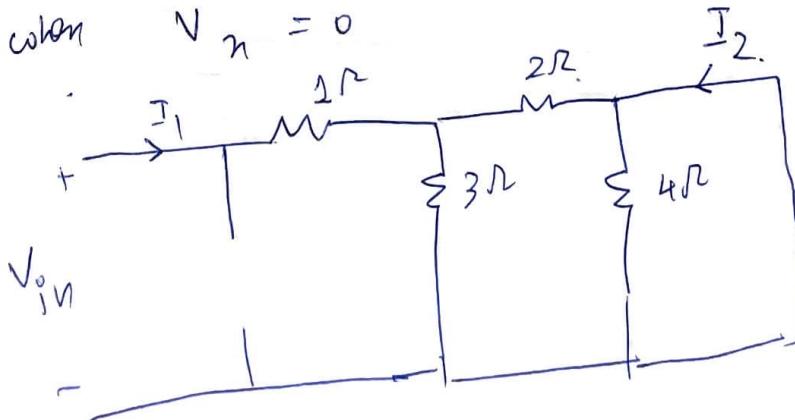

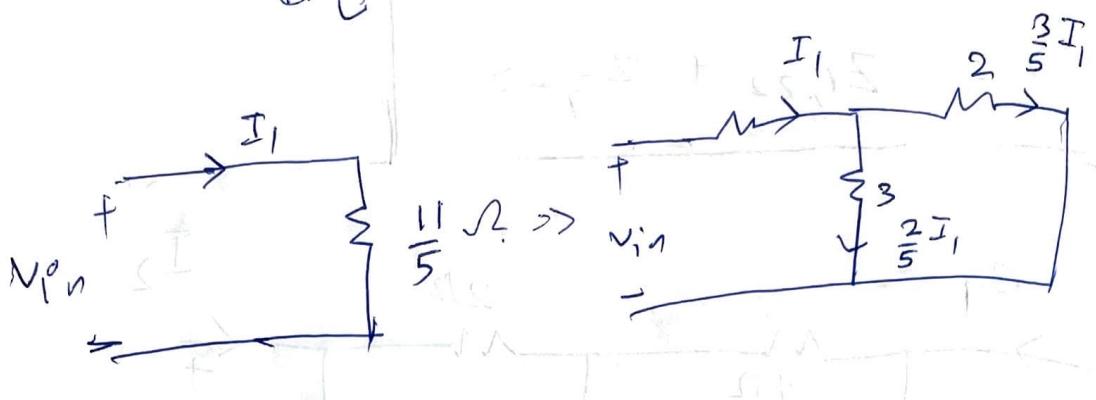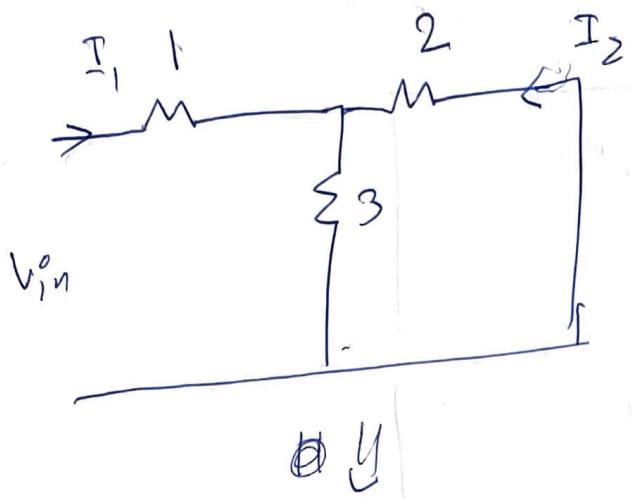

$$I_1 = \frac{5V_{in}}{11}$$

$$I_2 = \frac{3}{11} V_{in}$$



$$I_2 = Y_{21} V_{in}$$

$$I_1 = Y_{11} V_{in}$$

$$\frac{5V_{in}}{11} = Y_{11} V_{in} \quad \text{and} \quad \frac{3}{11} V_{in} = Y_{21} V_{in}$$

$$Y_{11} = \frac{5}{11} \quad ; \quad Y_{21} = \frac{3}{11}$$

$$V_{in} = 0$$

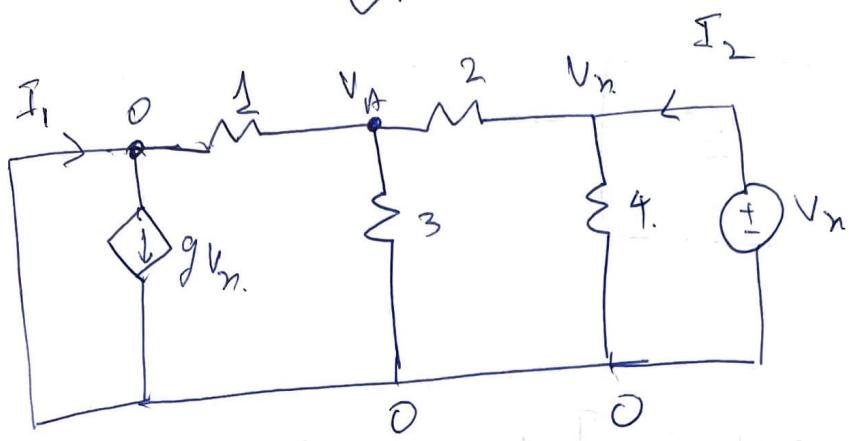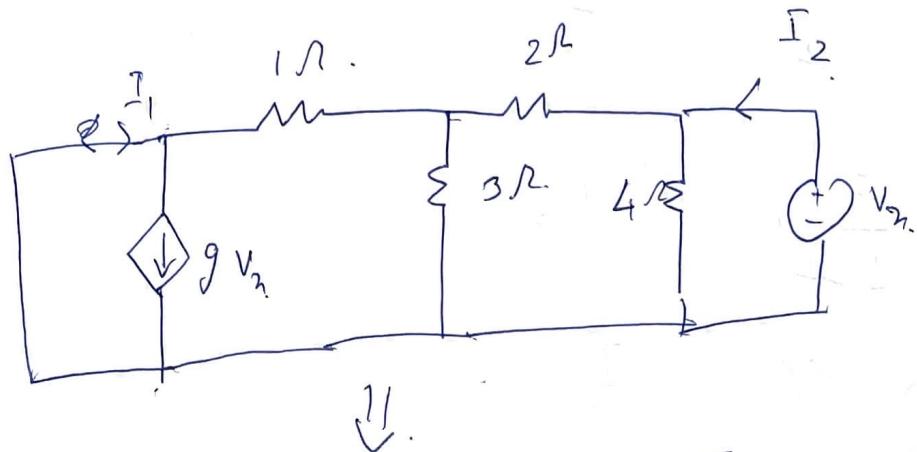

$$\frac{V_A}{3} + \frac{V_A}{1} + \frac{V_A}{2} = V_n = 0 \quad (1)$$

$$\frac{V_n - V_A}{2} + \frac{V_n}{4} = \pm I_2 = -(1)$$

$$\frac{0 - V_A}{1} + g V_n = \pm I_1 \quad (2)$$

$$\frac{V_A}{3} + V_A + \frac{V_A}{2} = \frac{V_n}{2} \Rightarrow \frac{11V_A}{6} = \frac{V_n}{2}$$

$$\Rightarrow \frac{11}{6} V_A = \frac{V_n}{2} \Rightarrow$$

$$\boxed{V_A = \frac{3V_n}{11}}$$

$$\cancel{\textcircled{1}} \quad \frac{V_y}{2} + \frac{V_y}{5} - \frac{V_A}{2} = I_2$$

$$\frac{3V_y}{4} - \frac{3V_y}{22} = I_2$$

$$\frac{27}{54} V_y = I_2$$

$$\frac{V_y}{4 \times 22}$$

$$\frac{27}{2}$$

$$I_2 = \frac{27}{44} V_n$$

$$-V_A + g V_n = I_1$$

$$-\frac{3}{11} V_n + g V_n = I_1$$

$$I_1 = V_n \left[g - \frac{3}{11} \right]$$


$$I_1 = \gamma_{12} V_n \Rightarrow \gamma_{12} = g - \frac{3}{11}$$

$$I_2 = \gamma_{22} V_n \quad \gamma_{22} = \frac{27}{44}$$

$$\gamma = \begin{bmatrix} \frac{5}{11} & g - \frac{3}{11} \\ \frac{3}{11} & \frac{27}{44} \end{bmatrix}$$

(b) for the ~~bottom to top~~ network to be unilateral one of the off diagonal elements ~~etc~~ should be zero so γ_{12} or γ_{21} need to be zero

$$\therefore g = \frac{3}{11}$$

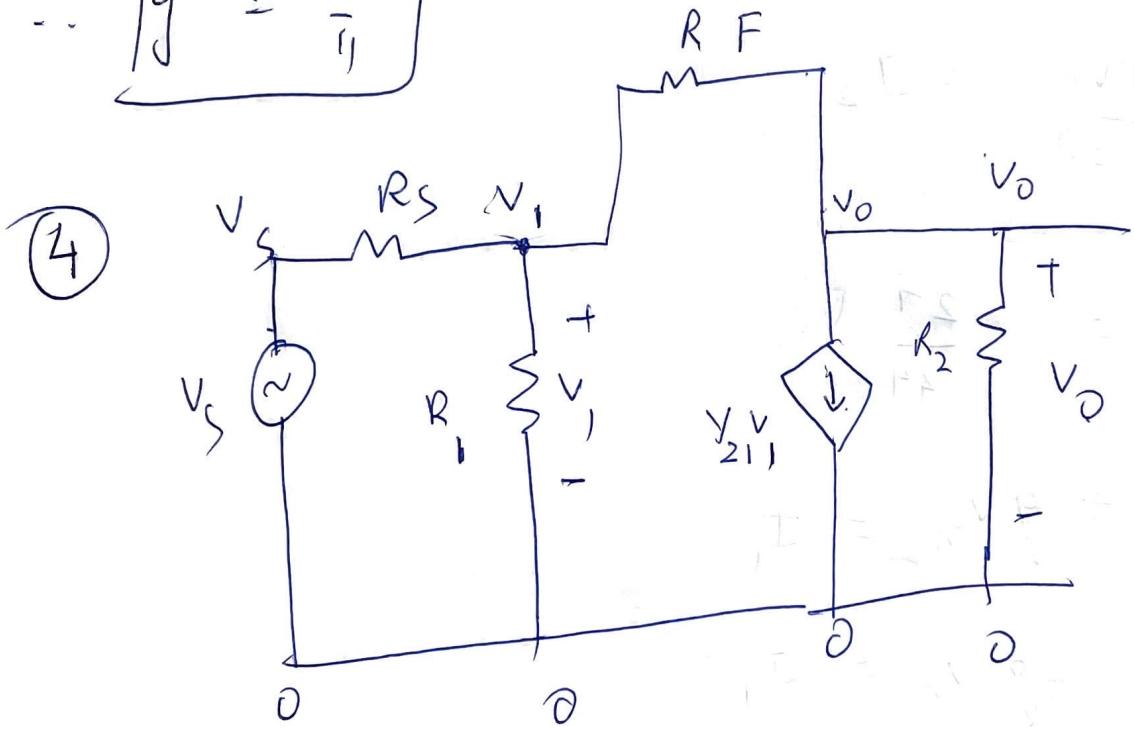

Nodal analysis

$$\frac{V_1}{R_1} + \frac{V_1 - V_S}{R_S} + \frac{V_1 - V_O}{R_F} = 0$$

$$\frac{V_0 - V_1}{R_F} + \frac{V_1}{R_2} + \frac{V_0}{R_F} = 0$$

$$\frac{V_0}{R_F} + \frac{V_0}{R_2} = \frac{V_1}{R_F} - \frac{V_1}{R_2} = 0$$

$$\frac{V_0}{R_F} + \frac{V_0}{R_2} = V_1 \left[\frac{1}{R_F} - \frac{1}{R_2} \right]$$

$$V_0 \left[\frac{1}{R_F} + \frac{1}{R_2} \right] = V_1 \left[\frac{1}{R_F} - \frac{1}{R_2} \right]$$

$$\frac{V_1}{R_1} + \frac{V_1}{R_S} + \frac{V_1}{R_F} = \frac{V_S}{R_S} + \frac{V_0}{R_F}$$

$$V_1 \left[\frac{R_S R_F + R_1 R_F + R_1 R_S}{R_1 R_S R_F} \right] = \frac{V_S}{R_S} + \frac{V_0}{R_F}$$

$$\frac{V_0 [R_F + R_2]}{R_2 [1 - R_F Y_{21}]} \frac{[R_S R_F + R_1 R_F + R_1 R_S]}{R_1 R_S R_F} - \frac{V_0}{R_F} = \frac{V_S}{R_S}$$

$$\frac{V_0 [R_F + R_2] [R_S R_F + R_1 R_F + R_1 R_S]}{R_2 [1 - R_F Y_{21}] R_1 R_S R_F} - \cancel{R_2 [1 - R_F Y_{21}] R_1 R_S R_F} = \frac{V_S}{R_S}$$

$$(a) \frac{V_o}{V_s} = \frac{R_2 [1 - R_F Y_{21}] R_1}{[R_F + R_2] [R_S R_F + R_S R_1 + R_F R_1] - [Y_{11} - Y_{21}] R_1 R_S}$$

$$(b) \frac{V_o}{V_s} = Y_{21} \left[R_2 \left(\frac{1}{Y_{21}} - R_F \right) R_1 \right]$$

$$Y_{21} \left[\frac{R_F + R_2}{R_F + R_2 + R_S R_F + R_S R_1 + R_F R_1} \right] - R_2 Y_{21} \left[\frac{1}{Y_{21}} - R_F \right] R_1 R_S$$

$$\frac{V_o}{V_s} = R_2 \left[\frac{1}{Y_{21}} - R_F \right] R_1 R_S$$

$$\lim_{Y_{21} \rightarrow \infty} \frac{[R_F + R_2] [R_S R_F + R_S R_1 + R_F R_1]}{Y_{21}} - R_2 \left[\frac{1}{Y_{21}} - R_F \right] R_1 R_S$$

$$= - \cancel{\frac{R_F + R_2}{R_F + R_2 + R_S R_F + R_S R_1 + R_F R_1}} = 0$$

$$+ \cancel{\frac{R_F R_S R_1}{R_F + R_S R_F + R_S R_1 + R_F R_1}}$$

$$- \frac{R_2 R_F R_1}{R_S R_L R_1} = \boxed{-\frac{R_F}{R_S}}$$